
 


Equivalent Decoder in Discrete Logic


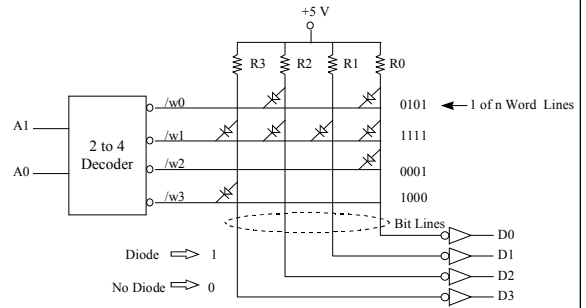


Internal Structure of 4x4 Diode ROM




Why use diodes?
Why not replace them with wires?

64 x 1 ROM with 2-Dimensional Decoding

  


64K x 8 ROM with 2-D Decoding

 


Is this a square chip?

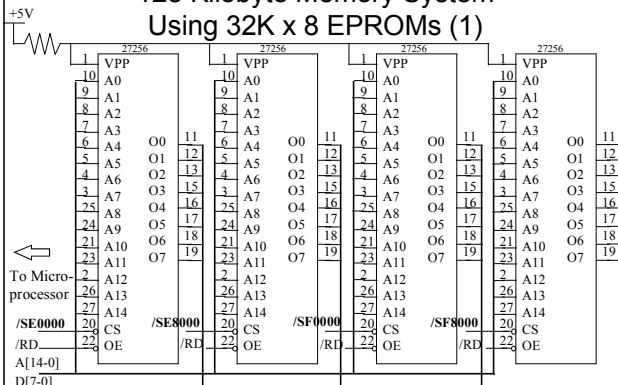128 Kilobyte Memory System Using 32K x 8 EPROMs (1)




Basic Structure of SRAM

 


- Address/Control/Data Out lines like a ROM (Reading)
+ Write Enable (WE) and Data In (DIN) (Writing)

One Bit of SRAM

 


- SEL and WR asserted → IN data stored in D-latch (Write)
- SEL only asserted → D-latch output enabled (Read)
- SEL not asserted → No operation

8 x 4 SRAM

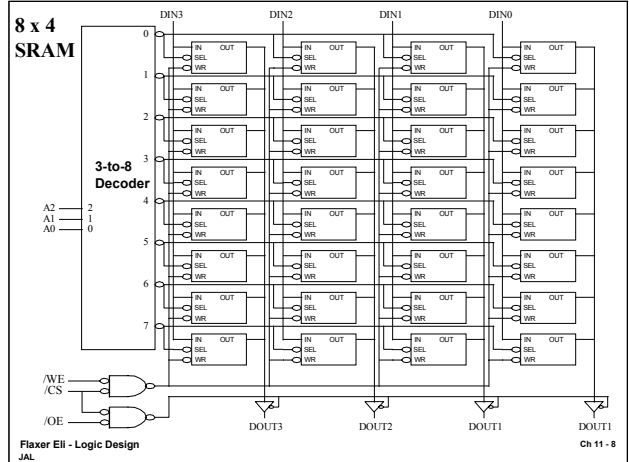


READ Timing (SRAM)

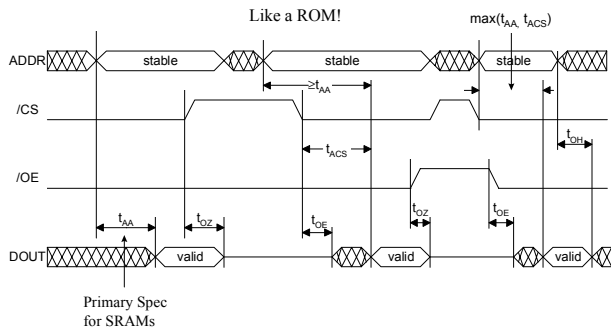


Primary Spec
for SRAMs

WRITE Timing (SRAM)

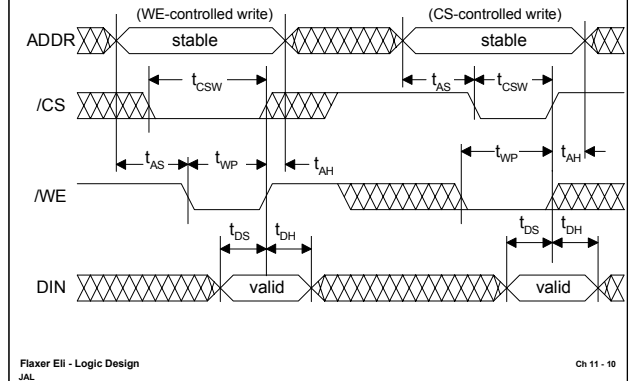

Physical SRAM Array Should Be Square

Example: 16 x 1 SRAM →
4 x 4 Array

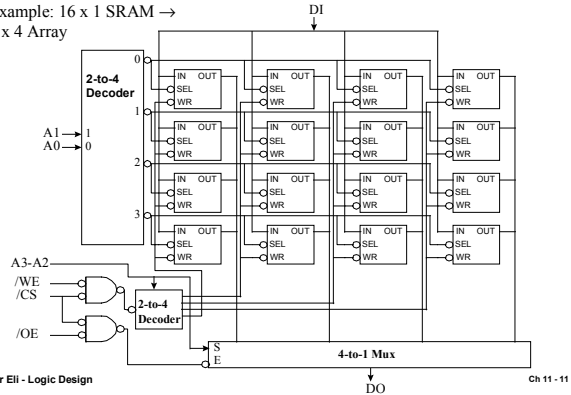

SRAM with Bidirectional Data Bus

