

Chapter 4

Memory

Process Control

Outline

➔ ● Read-Only Memory (ROM)


- Internal Structure
- Control and Timing

● Static RAM (SRAM)

- Internal Structure
- Control and Timing


● Dynamic RAM (DRAM)

 - Internal Structure
- Control and Timing



Read-Only Memory (ROM)

 - A combinational circuit with n inputs and b outputs:




- Programmable — values determined by user
- Nonvolatile — contents retained without power

Types Of ROMs (1)


- Mask ROM

 - Connections made by the semiconductor vendor
- Expensive setup cost
- Several weeks for delivery
- High volume only
- Bipolar or MOS technology



- PROM

 
- Programmable ROM
- Connections made by equipment manufacturer
- Vaporize (blow) fusible links with PROM programmer using high voltage/current pulses
- Bipolar technology
- One-time programmable



Types of ROMs (2)


- EPROM

 - Erasable Programmable ROM
- Charge trapped on extra “floating gate” of MOS transistors
- Exposure to UV light removes charge
 - 10-20 minutes
 - Quartz Lid = expensive package
- Limited number of erasures (10-100)



- EEPROM (E²ROM)

 - Electrically Erasable ROM
- Floating gates charged/discharged electrically
- Not RAM! (relatively slow charge/discharge)
- limited number of charge/discharge cycles (10,000)




Types of ROMs (3)

- Flash Memory


- Electronically erasable in blocks
- 100,000 erase cycles
- Simpler and denser than EEPROM

Outline

 - Read-Only Memory (ROM)
 - Internal Structure
 - **Control and Timing**
- ➔ ● Static RAM (SRAM)
 - Internal Structure
 - Control and Timing
- Dynamic RAM (DRAM)
 - Internal Structure
 - Control and Timing




Basic Structure of SRAM

 


- Address/Control/Data Out lines like a ROM (Reading)
 - + Write Enable (WE) and Data In (DIN) (Writing)

One Bit of SRAM

 


- SEL and WR asserted → IN data stored in D-latch (Write)
- SEL only asserted → D-latch output enabled (Read)
- SEL not asserted → No operation

READ Timing (SRAM)

 

WRITE Timing (SRAM)

 

RAM Summary

SRAM:

- Fast
- Simple Interface
- Moderate bit density (4 gates → 4 to 6 transistors)
- Moderate cost/bit

} Small systems
or
very fast
applications
(cache memory)

DRAM (Dynamic RAM):

- moderate speed
- complex interface
- High bit density (1 transistor cell)
- Low cost/bit

} Large Memories:
PC's
Mainframes